
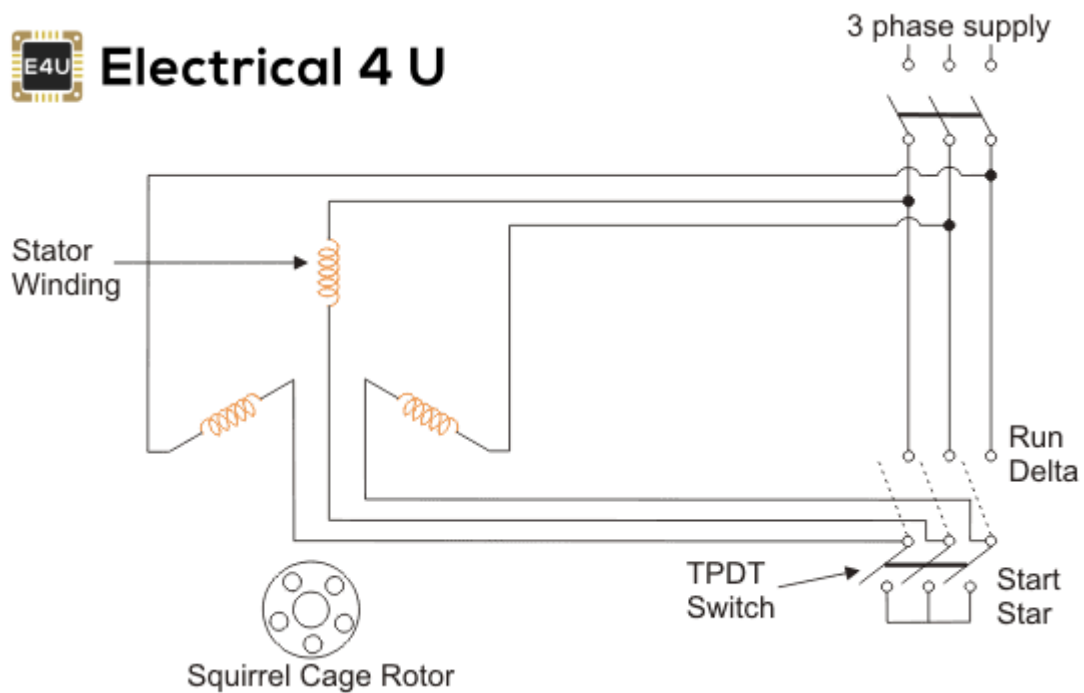


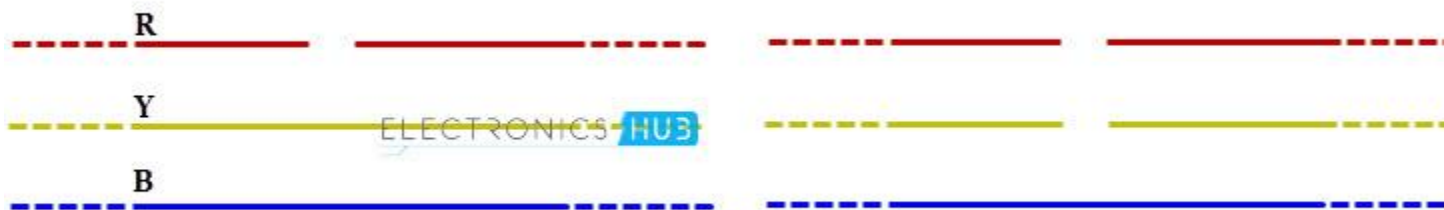

## Electrical 4 U



### Open-circuit Faults





(a). Single-phase open-circuit

(a). Two-phase open-circuit



(a). Three-phase open-circuit

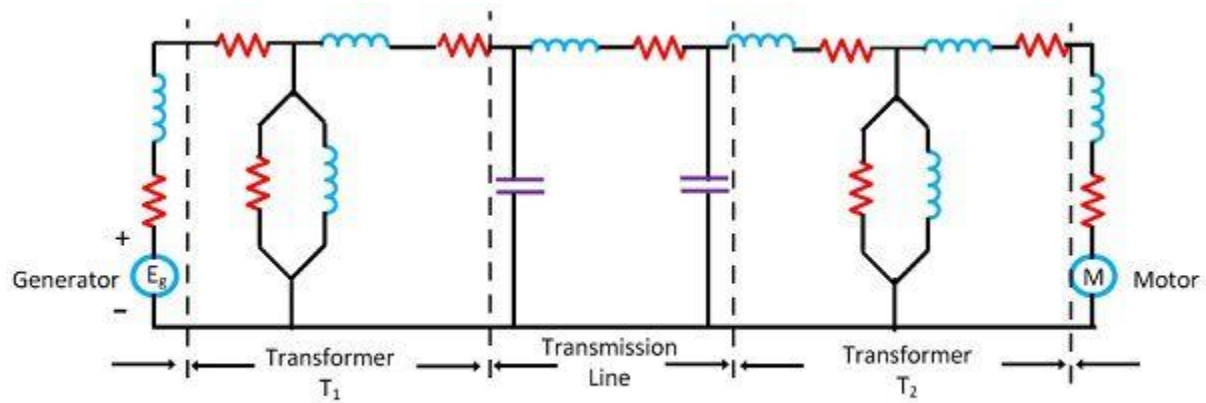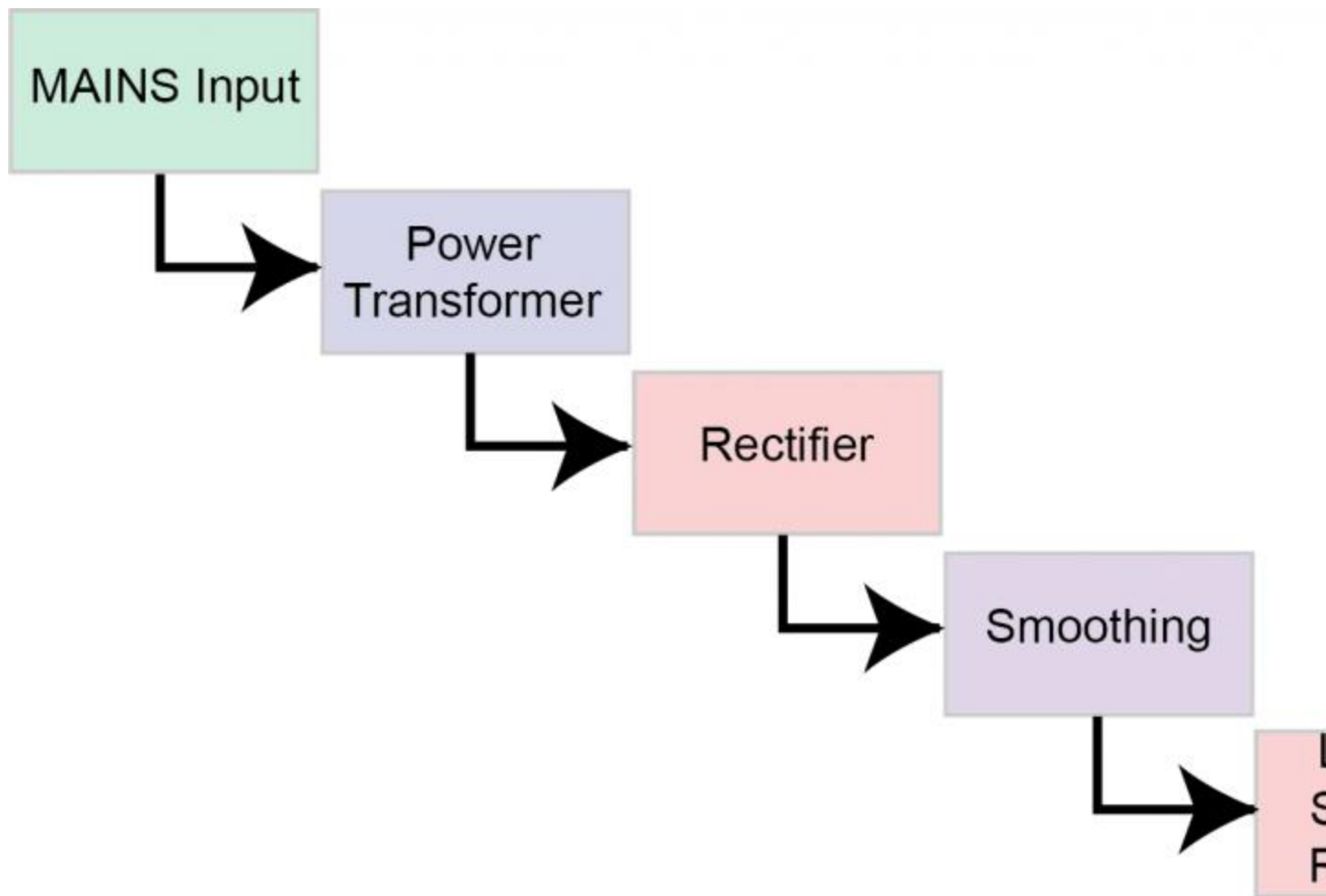

**Impedance Diagram For The Power System**

